

Q1) What are universal gates & why they are called as universal gates?

Q2) State and prove De-morgan's Theorem.

Q3) Explain universal gates with truth table

Q4) Explain Basic gates with truth table

Q5) Explain Exclusive gates with truth tables

Q6) Reduce the expression $f = \overline{AB + \bar{A} + AB}$

Q7) Apply De-morgan's Theorem to the expression

$$f = \overline{AB(CD + \bar{E}F)(\bar{A}B + \bar{C}D)}$$

Q8) De-morganize $f = \overline{(A + \bar{B})(C + D)}$

Q9) Reduce the expression $f = A[B + \bar{C}(\overline{AB + A\bar{C}})]$

Q10) Reduce the expression $f = A + B[AC + (B + \bar{C})D]$

Q11) Reduce the expression $f = \overline{(A + \bar{B}C)(A\bar{B} + ABC)}$

Q12) Reduce the expression $f = (B + BC)(B + \bar{B}C)(B + D)$

Q13) Reduce the expression $f =$

Show that

$$AB + A\bar{B}C + B\bar{C} = AC + B\bar{C}$$

14) Design a circuit using gates to realise the following functions

14.1) $Y = (A+BC)(B+\bar{C}A)$

14.2) $Y = \bar{A}\bar{B} \cdot \bar{A}\bar{C} \cdot \bar{B}\bar{C}$

14.3) $Y = \overline{(A+B)} + \overline{(A+C)} + \overline{(B+\bar{C})}$

14.4) $Y = BC + A\bar{C}$

14.5) $Y = (A+C) \cdot (B+\bar{C})$

K-map Q. No 15

15.1) Design a logic circuit using minimum number of basic gates for the following Boolean expression

$$f = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + \bar{A}BCD + AB\bar{C}\bar{D} + AB\bar{C}D + ABC\bar{D} + ABCD$$

15.2) Simplify the Boolean expression using K-map
 $f = \bar{A} + AB + ABD + A\bar{B}D + C$

15.3) Obtain the simplified expression using K-map

15.5) $f = \bar{A}\bar{B}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}BD + AB\bar{C}D$

15.4) Obtain the simplified expression using K-map

$$f = ABD + \bar{A}\bar{C}\bar{D} + \bar{A}B + \bar{A}\bar{C}\bar{D} + A\bar{B}D$$

Obtain the simplified expression using K-map

$$f = AB + A\bar{C} + C + AD + ABC + A\bar{B}C$$

- 16.1) Expand $\bar{A} + \bar{B}$ to minterms and maxterms
- 16.3) Expand $A + B\bar{C} + ABD + ABCD$ to minterms and maxterms
- 16.4) Expand $A(\bar{B} + A)B$ to minterms and maxterms.
- 16.5) Expand $A(\bar{A} + B)(\bar{A} + B + \bar{C})$ to minterms and maxterms
- 16.6) Expand $AB + A\bar{C} + BC$ into canonical SOP form
- 16.3) Expand $(A + B)(A + C)(B + \bar{C})$ into canonical POS form.

17.1) Reduce using mapping the expression

$$f = \sum m(2, 3, 6, 7, 8, 10, 11, 13, 14).$$

17.2) Reduce using mapping the expression

$$f = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 10, 12, 13).$$

and implement the real minimal expression in universal logic.

17.3) Reduce ~~to~~ using mapping the expression

$$f = \sum m(0, 1, 3, 4, 5, 6, 7, 13, 15)$$

and implement the real minimal expression in universal logic.

17.4) Reduce using mapping the following expression and implement the real minimal expression in universal logic.

$$f = \sum m(0, 2, 4, 6, 7, 8, 10, 12, 13, 15).$$

17.5) minimise the four variable logic function using K-map

$$f(A, B, C, D) = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 11, 14).$$

Don't care terms in K-map **Q. No-18**

18.1) Reduce the expression

$$f = \sum m(1, 5, 6, 12, 13, 14) + d(2, 4).$$

minimize the following expression using K-map

18.2) $f(A, B, C, D) = \sum m(1, 4, 7, 10, 13) + \sum d(5, 14, 15)$

18.3) $f(A, B, C, D) = \sum m(4, 5, 7, 12, 14) + \sum d(3, 8, 10)$

18.4) $f(W, X, Y, Z) = \sum m(1, 3, 7, 11, 15) + \sum d(0, 2, 5)$

18.5) $f(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 5) + d(10, 11, 12, 13, 14, 15)$

K-map

POS form

Q.No- 19

19.1) Reduce using mapping the expression

$f = \Pi m(4, 6, 11, 14, 15)$ and implement the real minimal expression in universal logic.

19.2) Reduce using mapping the expression

$f = \Pi m(2, 8, 9, 10, 11, 12, 14)$. and implement the real minimal expression in universal logic.

19.3) Reduce using mapping the following expression and implement the real minimal expression in universal logic

$$f = \Pi m(\cancel{0, 2, 4, 6, 7, 8}, f = \Pi m(1, 3, 5, 9, 11, 14).$$

minimize the following expression using k-map

19.4) $F(A, B, C, D) = \Pi m(0, 3, 7, 8, 9, 10, 11, 15) \cdot \Pi d(2, 4)$.

19.5) $F(A, B, C, D) = \Pi m(6, 7, 8, 9) \cdot d(10, 11, 12, 13, 14, 15)$.