

NMDC DAV Polytechnic Dantewada.

Digital Electronics IMP Questions

4th Semester

- 1) What are the difference between Digital System and Analog System?
- 2) Define digital System. Write the advantage of digital system over Analog system.
- 3) What are the number systems and codes in digital electronics. Explain alpha-numeric, weighted and non-weighted codes.
- 4) State and prove De-Morgan's theorem with example.
- 5) What do you mean by Universal gate? what are they? Why are they called Universal gates?
- 6) Explain BCD to seven segment decoder with complete working
- 7) What do you mean by multiplexer? Design 1x8 MUX using logic gates.
- 8) What do you mean by De-multiplexer? Design 8x1 De-MUX using logic gates.
- 9) Difference between multiplexer and demultiplexer.
- 10) What is difference between decoder and demultiplexer.
- 11) Explain 3 line to 8 line decoder, with the help of a logic diagram and a truth table.
- 12) Explain Full adder using 2 half adder with truth table and block diagram .
- 13) Explain Full subtractor using 2 half subtractor with truth table and block diagram .
- 14) Explain S-R Flip-flop. Also derive the excitation table and characteristic equation of the same.
- 15) What is 'Race around condition'? How race around can be eliminated?
- 16) Explain in brief a master-slave flip-flop.
- 17) Explain IC 7490 with pin diagram, truth table and its application.
- 18) Explain IC 74151 with pin diagram, truth table and its application.
- 19) What is shift register ? explain different types shift register with the help of a neat diagram.
- 20) Write the working of a J.K Flip-flop using NAND gate along with its logic diagram, characteristic equation.
- 21) Distinguish between EEPROM and UVROM.
- 22) Explain weighted resistor D/A converter with neat diagram
- 23) Explain R-2R ladder type D/A converter with examples.
- 24) Explain Dual-slope A/D converter with neat diagram.
- 25) Successive approximation type A/D converter with a proper diagram.
- 26) Explain the following:-
 - 1) EPROM
 - 2) PRROM
 - 3) Volatile memory
 - 4) Static RAM
 - 5) Dynamic RAM
 - 6) Semiconductor memories
 - 7) Flash memories
 - 8) RAM
 - 9) ROM
 - 10) EEPROM
 - 11) UVEPROM
 - 12) Flash ROM